Shane Riley programmer wires not shown) 14 / PB0 220 [Ω] LĖD 0 15 / PB1 220 [Ω] LED 1 +5 V 16 / PB2 220 [Ω] LED 2 17 / PB3 220 [Ω] LĖD 3 18 / PB4 220 [Ω] LED 4 +5 V 50 [kΩ] 23 / PC0

(Controller, oscillator,

Lab 4