(Controller, oscillator, Shane Riley programmer wires not shown) 23 / PC0 $220 [\Omega]$ LĖD 0 24 / PC1 220 [Ω] LED 1 +5 V 25 / PC2 220 [Ω] LĖD 2 26 / PC3 220 [Ω] LED 3 10 [kΩ] 4 / INTO **GND** 10 [kΩ] +5 V 5 / INT1 GND

Lab 3